

MIPS CPU Project Report

1. Instruction Analysis

00221820	add: R3, R1, R2	
AC010000	sw: R1, 0(R0)	
8C240000	lw R4, 0(R1)	
10210001	beq R1, R1, +8	//Branch taken
00001820	add R3, R0, R0	//This instruction will be skipped because of branch taken
00411822	sub R3, R2, R1	

All the instruction was assigned at the “Instruction.tex”

2. Simulation

The register file was be initially by assigned

R0 = 0;

R1 = 8;

R2 = 20

The instruction memory was be initially assigned

Mem[0] = 5;


Mem[1] = 6;

Mem[2] = 7;

So we could conclude all the signals as follow:

clock	1	2	3	4	5
PCout	4	8	12	16	24
inst	00221820	AC010000	8C240000	10210001	00411822
ReadData1	8	0	8	8	20
ReadData2	20	8	0	8	8
ALUout	28	0	8	0	12
ReadData	-	-	7	-	-
WriteReg	R3	R1	R4	R1	R3

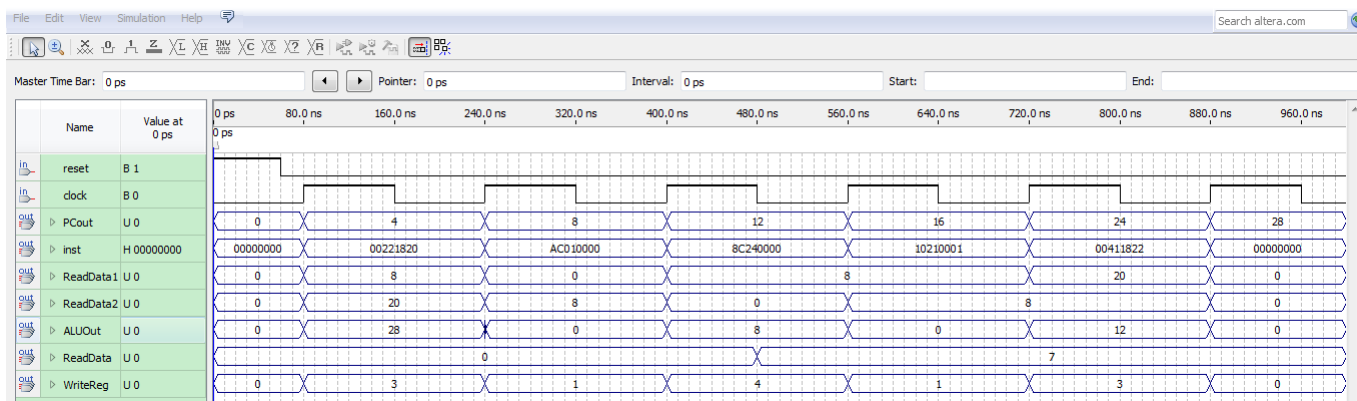Note the 3rd clock cycle is LW instruction, so the ReadData from DataMemory was 7, ALUout = 8 means the word address was Mem[2]. And all of the other computing results were right. The waveform is as follow:



3. Source Design Code

3.1 PC

```
module PC(clock, reset, PCin, PCout);

input clock, reset;
input [31:0] PCin;

output reg [31:0] PCout;

always @(posedge clock) begin
    if (reset == 1)
        PCout <= 0;
    else
        PCout <= PCin + 4;
end
endmodule
```

3.2 Instruction Memory

```
module InstMem(clock, address, inst);

input clock;
input [31:0] address;

output reg [31:0] inst;

reg [31:0] Mem [0:127];

initial begin
    $readmemh("Instruction.txt", Mem, 0, 5);
end

always @(posedge clock) begin
    inst <= Mem[address[31:2]];
end
endmodule
```

3.3 Main Control

```
module MainControl(
input [5:0] Opcode,

output reg RegDst, RegWrite, ALUSrc,
output reg MemtoReg, MemRead, MemWrite,
output reg Branch,
```

Single Clock Cycle MIPS CPU

output reg [1:0] ALUOp);

always @(*) begin

case(Opcode)

0: begin

RegDst <= 1;
ALUSrc <= 0;
MemtoReg <= 0;
RegWrite <= 1;
MemRead <= 0;
MemWrite <= 0;
Branch <= 0;
ALUOp <= 2'b10;;

end

35: begin

RegDst <= 0;
ALUSrc <= 1;
MemtoReg <= 1;
RegWrite <= 1;
MemRead <= 1;
MemWrite <= 0;
Branch <= 0;
ALUOp <= 2'b00;;

end

43: begin

RegDst <= 0;
ALUSrc <= 1;
MemtoReg <= 0;
RegWrite <= 0;
MemRead <= 0;
MemWrite <= 1;
Branch <= 0;
ALUOp <= 2'b00;

end

4: begin

RegDst <= 0;
ALUSrc <= 0;
MemtoReg <= 0;
RegWrite <= 0;
MemRead <= 0;
MemWrite <= 0;
Branch <= 1;
ALUOp <= 2'b01;

end

endcase

end

endmodule

3.4 Mux1 (For instMem to RegFile)

```
module Mux1(inst20_16, inst15_11, RegDst, WriteReg);

input [20:16] inst20_16;
input [15:11] inst15_11;
input RegDst;

output reg [4:0] WriteReg;

always @ (RegDst, inst20_16, inst15_11) begin
    case(RegDst)
        0 : WriteReg <= inst20_16;
        1 : WriteReg <= inst15_11;
    endcase
end
endmodule
```

3.5 ALU Control

```
module ALUControl (ALUOp, FuncCode, ALUCtl);

input [1:0] ALUOp;
input [5:0] FuncCode;
output reg [3:0] ALUCtl;

always @(ALUOp, FuncCode) begin
    if(ALUOp == 0)
        ALUCtl <= 2;    //LW and SW use add
    else if(ALUOp == 1)
        ALUCtl <= 6;    // branch use subtract
    else
        case(FuncCode)
            32: ALUCtl <= 2; //add
            34: ALUCtl <= 6; //subtract
            36: ALUCtl <= 0; //and
            37: ALUCtl <= 1; //or
            39: ALUCtl <= 12; //nor
            42: ALUCtl <= 7; //slt
            default: ALUCtl <= 15; //should not happen
        endcase
    end
end
endmodule
```

3.6 Mux2

```
module Mux2 (ALUSrc, ReadData2, Extend32, ALU_B);

input ALUSrc;
input [31:0] ReadData2, Extend32;

output reg [31:0] ALU_B;

always @(ALUSrc, ReadData2, Extend32) begin
    case (ALUSrc)
        0: ALU_B <= ReadData2 ;
        1: ALU_B <= Extend32;
    endcase
end
endmodule
```

3.7 Register File

```
module RegFile(clock, RegWrite, ReadReg1, ReadReg2, WriteReg, WriteData, ReadData1, ReadData2);

input clock;
input RegWrite;

input [4:0] ReadReg1, ReadReg2, WriteReg;
input [31:0] WriteData;

output [31:0] ReadData1, ReadData2;

reg [31:0] reg_mem [0:31];
initial begin
    reg_mem[0] <= 0;
    reg_mem[1] <= 8;
    reg_mem[2] <= 20;
end
assign ReadData1 = reg_mem[ReadReg1];
assign ReadData2 = reg_mem[ReadReg2];

always @(posedge clock) begin
    if (RegWrite == 1)
        reg_mem[WriteReg] = WriteData;
end
endmodule
```

3.8 ALU

```
module ALU (ALUCtl, A, B, ALUOut, Zero);

input [3:0] ALUCtl;
```

```
input [31:0] A,B;

output reg [31:0] ALUOut;
output Zero;
assign Zero = (ALUOut == 0);

always @(ALUCtl, A, B) begin
    case (ALUCtl)
        0: ALUOut <= A & B;
        1: ALUOut <= A | B;
        2: ALUOut <= A + B;
        6: ALUOut <= A - B;
        7: ALUOut <= A < B ? 1:0;
        12: ALUOut <= ~(A | B);
        default: ALUOut <= 0;
    endcase
end
endmodule
```

3.9 Sign Extend

```
module SignExtend (inst15_0, Extend32);

input [15:0] inst15_0;
output reg [31:0] Extend32;

always @(inst15_0) begin
    Extend32[31:0] <= inst15_0[15:0];
end
endmodule
```

3.10 Shift Left 2

```
module ShiftLeft2 (ShiftIn, ShiftOut);

input [31:0] ShiftIn;
output reg [31:0] ShiftOut;

always @(ShiftIn) begin
    ShiftOut = ShiftIn << 2;
end

endmodule
```

3.11 Add_ALU

```
module Add_ALU(PCout, ShiftOut, Add_ALUOut);
```

```
input [31:0] PCout;
input [31:0] ShiftOut;

output reg [31:0] Add_ALUOut;

always @(*) begin
    Add_ALUOut <= PCout + ShiftOut;
end
endmodule
```

3.12 Mux4 (For Branch)

```
module Mux4 (PCout, Add_ALUOut, AndGateOut, PCin);

input [31:0] PCout, Add_ALUOut;
input AndGateOut;

output reg [31:0] PCin;

initial begin
    PCin <= 0;
end

always @(*) begin
    case (AndGateOut)
        0: PCin <= PCout ;
        1: PCin <= Add_ALUOut;
    endcase
end
endmodule
```

3.13 Data Memory

```
module DataMemory (clock, address, MemWrite, MemRead, WriteData, ReadData);

input clock;
input [6:0] address;
input MemWrite, MemRead;
input [31:0] WriteData;

output reg [31:0] ReadData;

reg [31:0] Mem[0:127]; //32 bits memory with 128 entries

initial begin
    Mem[0] = 5;
end
```

```
        Mem[1] = 6;
        Mem[2] = 7;
    end

    always @ (posedge clock) begin

        if (MemWrite == 1)
            Mem[address[6:2]] <= WriteData;
        end

        always @(negedge clock) begin
            if (MemRead == 1)
                ReadData <= Mem[address[6:2]];
            end
        end
    endmodule
```

3.14 Mux3 (For ALU)

```
module Mux3 (ReadData, ALUOut, MemtoReg, WriteData_Reg);

    input [31:0] ReadData, ALUOut;
    input MemtoReg;

    output reg [31:0] WriteData_Reg;

    always @(*) begin
        case (MemtoReg)
            0: WriteData_Reg <= ALUOut ;
            1: WriteData_Reg <= ReadData;
        endcase
    end
endmodule
```

3.15 And Gate

```
module AndGate(Branch, Zero, AndGateOut);

    input Branch;
    input Zero;
    output reg AndGateOut;

    always @(*) begin
        AndGateOut <= Branch && Zero;
    end
endmodule
```


3.16 MipsCPU

```
module MipsCPU(clock, reset,
               PCin,PCout,
               inst,
               RegDst, RegWrite, ALUSrc, MemtoReg, MemRead, MemWrite, Branch,
               ALUOp,
               WriteReg,
               ReadData1, ReadData2,
               Extend32,
               ALU_B,
               ShiftOut,
               ALUCtl,
               Zero,
               ALUOut,
               Add_ALUOut,
               AndGateOut,
               ReadData,
               WriteData_Reg);

input clock;
input reset;

//Connection of PC
output wire [31:0] PCin, PCout;
PC pc_0(
    //inputs
    .clock(clock),
    .reset(reset),
    .PCin(PCin),
    //outputs
    .PCout(PCout)
);

//Connection of InstMem
output wire [31:0] inst;
InstMem instmem_0(
    //inputs
    .clock(clock),
    .address(PCin),
    //outputs
    .inst(inst)
);

//Connection of MainControl
output wire RegDst, RegWrite, ALUSrc, MemtoReg, MemRead, MemWrite, Branch;
```

Single Clock Cycle MIPS CPU

```
output wire [1:0] ALUOp;
MainControl main_control_0(
    //inputs
    .Opcode(inst[31:26]),
    //outputs
    .RegDst(RegDst),
    .RegWrite(RegWrite),
    .ALUSrc(ALUSrc),
    .MemtoReg(MemtoReg),
    .MemRead(MemRead),
    .MemWrite(MemWrite),
    .Branch(Branch),
    .ALUOp(ALUOp)
);
```

//Connection of the Mux between InstMem and RegisterFile

```
output wire [4:0] WriteReg;
Mux1 mux1_0(
    //inputs
    .inst20_16(inst[20:16]),
    .inst15_11(inst[15:11]),
    .RegDst(RegDst),
    //outputs
    .WriteReg(WriteReg)
);
```

//Connection of RegFile

output wire [31:0] ReadData1, ReadData2;

```
RegFile regfile_0(
    //inputs
    .clock(clock),
    .ReadReg1(inst[25:21]),
    //*****
    .ReadReg2(inst[20:16]),
    .RegWrite(RegWrite),
    .WriteReg(WriteReg),
    .WriteData(WriteData_Reg),
    //outputs
    .ReadData1(ReadData1),
    .ReadData2(ReadData2)
);
```

//Connection of SignExtend

output wire [31:0] Extend32;

```
SignExtend sign_extend_0(
    //inputs
    .inst15_0(inst[15:0]),
```

```
//outputs
.Extend32(Extend32)
);

//Connection of Mux2
output wire [31:0] ALU_B;
Mux2 mux2_0(
    //inputs
    .ALUSrc(ALUSrc),
    .ReadData2(ReadData2),
    .Extend32(Extend32),
    //outputs
    .ALU_B(ALU_B)
);

//Connection of ShiftLeft2
output wire [31:0] ShiftOut;
ShiftLeft2 shift_left2_0(
    //inputs
    .ShiftIn(Extend32),
    //outputs
    .ShiftOut(ShiftOut)
);

//Connection of ALUControl
output wire [3:0] ALUCtl;
ALUControl alu_control_0(
    //inputs
    .ALUOp(ALUOp),
    .FuncCode(inst[5:0]),
    //outputs
    .ALUCtl(ALUCtl)
);

//Connection of ALU
output wire Zero;
output wire [31:0] ALUOut;
ALU alu_0(
    //inputs
    .A(ReadData1),
    .B(ALU_B),
    .ALUCtl(ALUCtl),
    //outputs
    .ALUOut(ALUOut),
    .Zero(Zero)
);
```

Single Clock Cycle MIPS CPU

```
//Connection of Add_ALU
output wire [31:0] Add_ALUOut;
Add_ALU add_alu_0(
    //inputs
    .PCout(PCout),
    .ShiftOut(ShiftOut),
    //outputs
    .Add_ALUOut(Add_ALUOut)
);
```

```
//Connection of AndGate
output wire AndGateOut;
AndGate and_gate_0(
    //inputs
    .Branch(Branch),
    .Zero(Zero),
    //outputs
    .AndGateOut(AndGateOut)
);
```

```
//Connection of Mux4
Mux4 mux4_0(
    //inputs
    .PCout(PCout),
    .Add_ALUOut(Add_ALUOut),
    .AndGateOut(AndGateOut),
    //outputs
    .PCin(PCin)
);
```

```
//Connection of DataMemory
output wire [31:0] ReadData;
DataMemory data_memory_0(
    //inputs
    .clock(clock),
    .address(ALUOut),
    .MemWrite(MemWrite),
    .MemRead(MemRead),
    .WriteData(ReadData2),
    //outputs
    .ReadData(ReadData)
);
```

```
//Connection of Mux3
output wire[31:0] WriteData_Reg;
Mux3 mu3_0(
    //inputs
```

Single Clock Cycle MIPS CPU

```
.ReadData(ReadData),  
.ALUOut(ALUOut),  
//outputs  
.WriteData_Reg(WriteData_Reg)  
);  
endmodule
```